21 Three capacitors are connected in the shape of a triangle ABC as shown in the figure below.

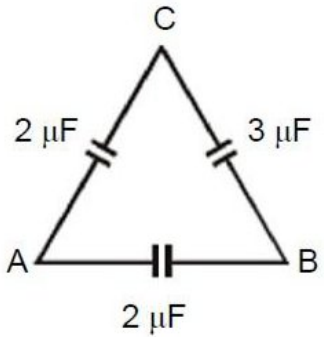

A 5.0 V battery is connected between A and B.

What is the voltage between B and C?

A 1.0 V **B** 2.0 V **C** 2.5 V **D** 3.0 V