		Resistance of the rod = V/I = 3.0/ 2.41 = 1.2 Ω
24	**A**	Intensity decreases ⇒ resistance of LDR increases. Total resistance of circuit increases, total current decreases. p.d. across fixed resistor decreases