21	**Ans: A** When the capacitors are connected in series with the cell of emf E, the total capacitance is $\frac{C}{3}$ and the total charge stored $Q_1 = \frac{CV}{3}$ When the capacitors are connected in parallel, the total capacitance is $3C$ and the total charge stored $Q_2 = 3CV$ Hence, $\frac{Q_1}{Q_2} = \frac{\frac{CV}{3}}{3CV} = \frac{1}{9}$