22	**Ans: A** Power dissipated, $P = \frac{V^2}{R}$ Since the resistors are identical, $P \propto V^2$ R and Q are connected in parallel, hence $V_S : V_R : V_Q$ or $V_S{}^2 : V_R{}^2 : V_Q{}^2$ 2 : 1 : 1 or 4 : 1 : 1 Power dissipated across R = $\frac{1}{6} \times 12$ = 2 W