23	**Ans: C** V_T is across the resistor, hence for the reading to be high, it means that the voltage across the thermistor is low. For the voltage across the thermistor to be low, its resistance is low which indicates that the temperature is high. * From notes: Commonly used thermistors have a *negative temperature coefficient*, i.e. resistance *decreases* as temperature *increases* V_L is across the LDR, hence for the reading to be high, its resistance is high which indicates that the light intensity is low. *From notes: Light-dependent resistors are semiconductors whose resistance *decreases* as light intensity falling on them *increases*.