23	**B**	When the resistance of variable resistor is reduced, the combined resistance of the external circuit is reduced. The total resistance in the circuit is reduced and the current is increased. With an increase in current, there is a larger potential drop across the internal resistance, therefore, the terminal potential difference (i.e. *V*) will decrease. The current in the external fixed resistor is decreased since the its p.d. decreased. Since the current through the e.m.f increases while the current through the external fixed resistor is decreased, the current in the variable resistor must increase.
24	**D**	*R* (1)