



resistor is decreased, the current in the variable resistor must increase.

24 **D**

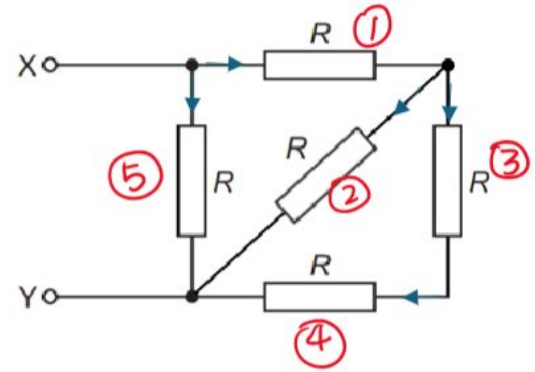

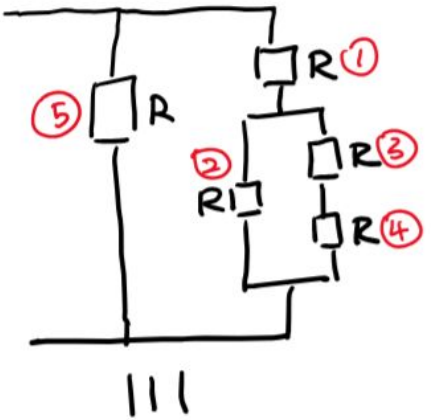

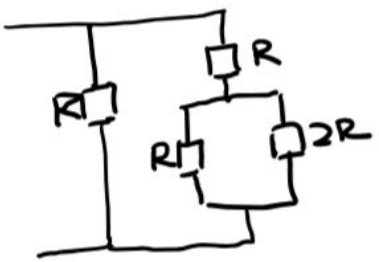

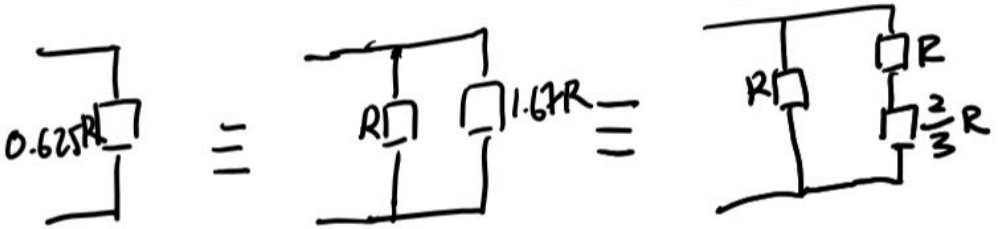

Total resistance = $0.625R$

$120 = 0.625R$

$R = 192\ \Omega$