21 A steady current I dissipates a certain power in a variable resistor. The resistance has to be halved to obtain the same power when a sinusoidal alternating current is used.

What is the r.m.s. value of the alternating current?

A $\frac{1}{2}I$ **B** $\sqrt{\frac{1}{2}}I$ **C** I **D** $\sqrt{2}I$