24 Five resistors, each of resistance R, are connected as shown.

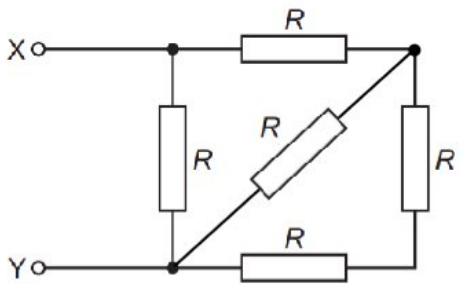

The total resistance between point X and point Y is 120 Ω.

What is the magnitude of the resistance R?

A 120 Ω **B** 150 Ω **C** 170 Ω **D** 190 Ω