23 Three identical capacitors are connected to a battery in three different arrangements as shown below.

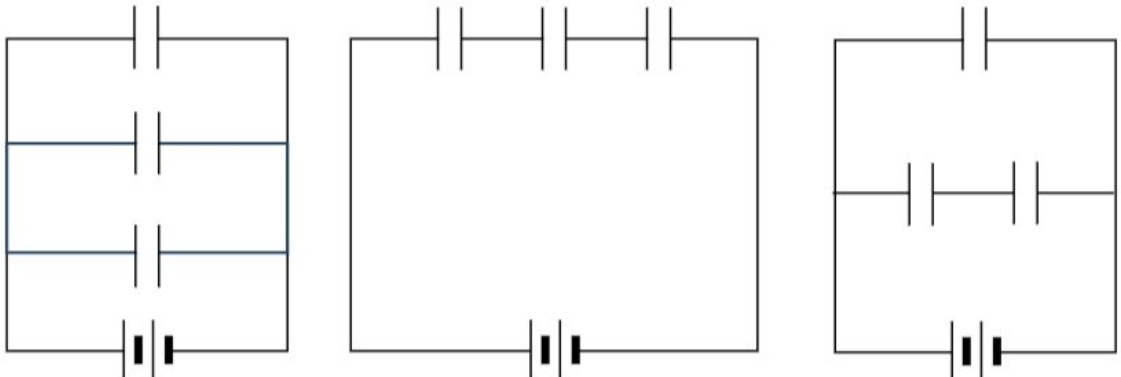

Which of the following lists the arrangements in order of increasing capacitance?

A PRQ **B** QRP **C** PQR **D** RQP