26 A generator produces a current of 60.0 A r.m.s at a voltage of 120 V r.m.s. An ideal transformer steps up the voltage to a peak value of 4500 V and transmits the power through a cable of total resistance 40.0 Ω to the consumers.

What is the percentage of power transmitted to the consumers?

A 94.3 %

B 97.2 %

C 98.6 %

D 99.3 %