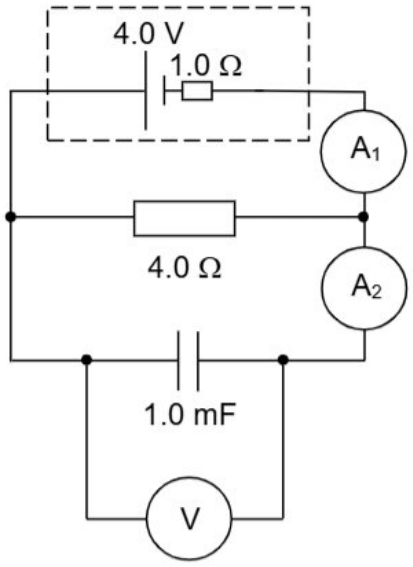
23 A battery of e.m.f. 4.0 V and internal resistance 1.0 Ω is connected to a 4.0 Ω resistor and 1.0 mF capacitor.



What are the readings of the voltmeter V and the ammeters A_1 and A_2 when the capacitor is fully charged?

	reading of V	reading of A_1	reading of A_2
A	3.0 V	0.8 A	0.2 A
B	3.2 V	0.8 A	0 A
C	3.2 V	1.0 A	0.2 A
D	4.0 V	0 A	0 A