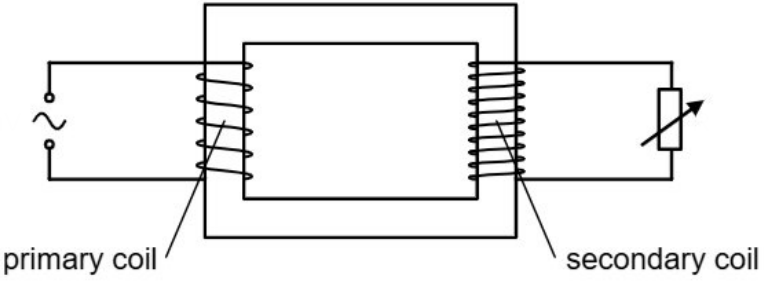
26 The primary coil of a transformer is connected to an alternating voltage supply. The secondary coil is connected across a variable resistor.



Which change will cause an increase in the p.d. across the secondary coil?

A decreasing the cross-sectional area of the secondary coil

B decreasing the current in the primary coil

C decreasing the resistance of the variable resistor

D decreasing the number of turns of the primary coil