25 The variation with time of an alternating current I_p connected to the primary coil of a transformer is as shown.

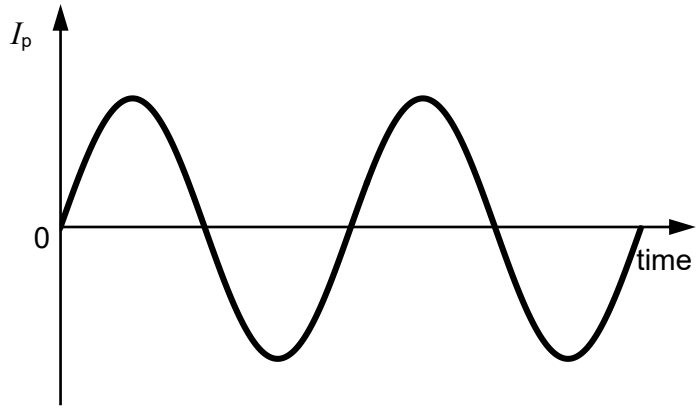

Which graph represents the variation with time of the power output, *P*, in a resistor connected across the secondary coil?

A

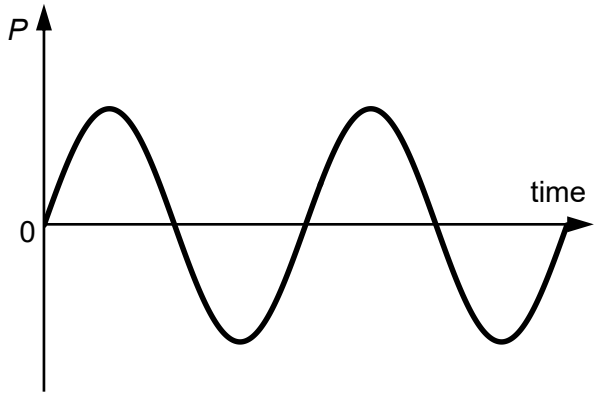

B

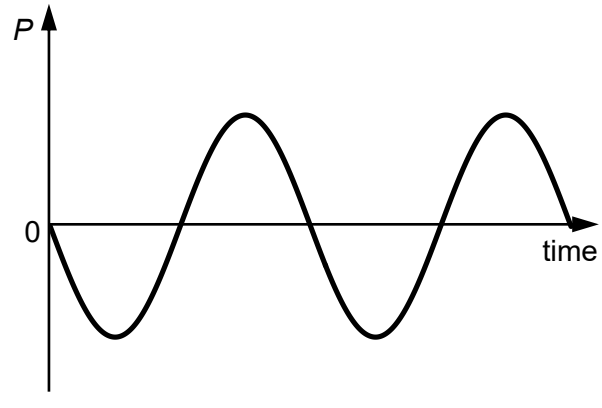

C

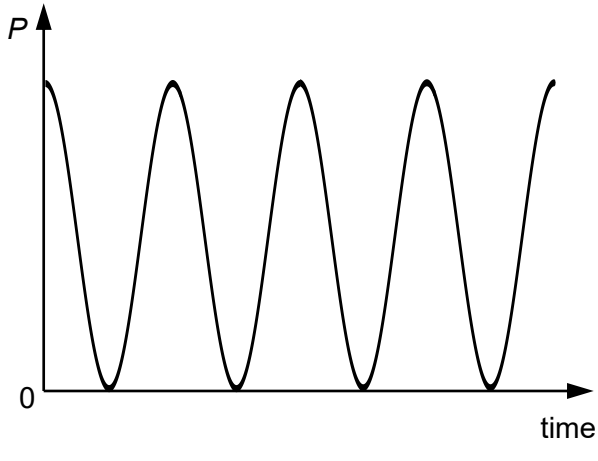
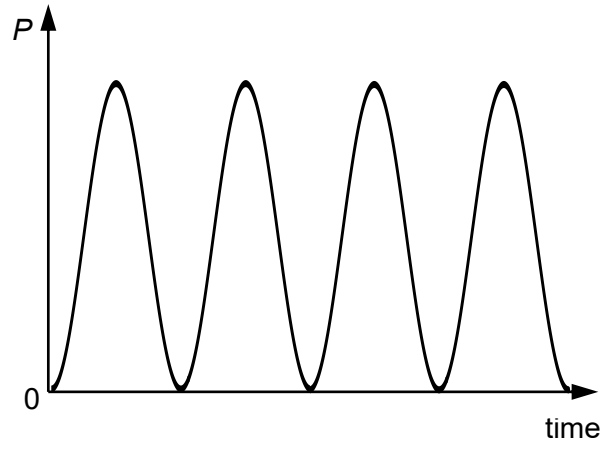
D