21 The diagram shows a network of 7 resistors, each with resistance R.

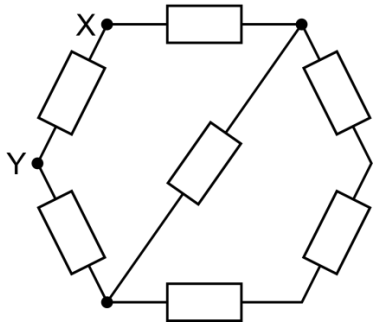

What is the resistance between points X and Y?

A $\frac{2}{3}R$ **B** $\frac{3}{5}R$ **C** $\frac{7}{11}R$ **D** $\frac{11}{15}R$