20 Three identical cells each having an e.m.f of 1.5 V and a constant internal resistance of 2.0 Ω are connected in series with a 4.0 Ω resistor *R*, firstly as in circuit (i), and secondly as in circuit (ii).

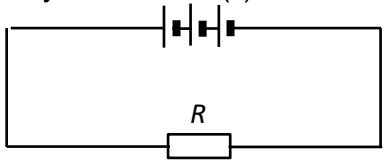

Circuit (i)

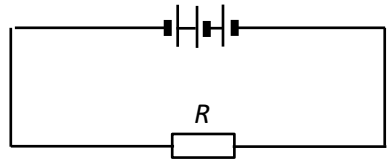

Circuit (ii)

What is the ratio $\frac{power\ in\ R\ in\ circuit\ (i)}{power\ in\ R\ in\ circuit\ (ii)}$?

A 9.0 **B** 7.2 **C** 5.4 **D** 3.0