22 An electric kettle, designed for travelers, can be used with different supply voltages. It is rated at 600 W for a 240 V r.m.s. alternating supply. What will be its power output if it is connected to a 120 V direct supply?

A 150 W **B** 300 W

C 600 W **D** 1.20 kW