20 The figure below shows some capacitors arranged between P and Q.

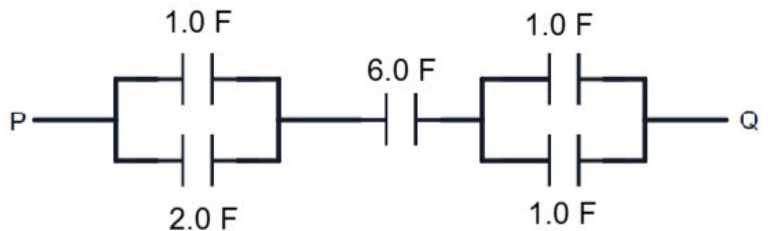

What is the total capacitance between points P and Q?

A 1.0 F B 7.0 F **C** 10 F **D** 11 F