22 The sinusoidal a.c. source shown in the circuit diagram below has a peak-to-peak voltage of 18 V.

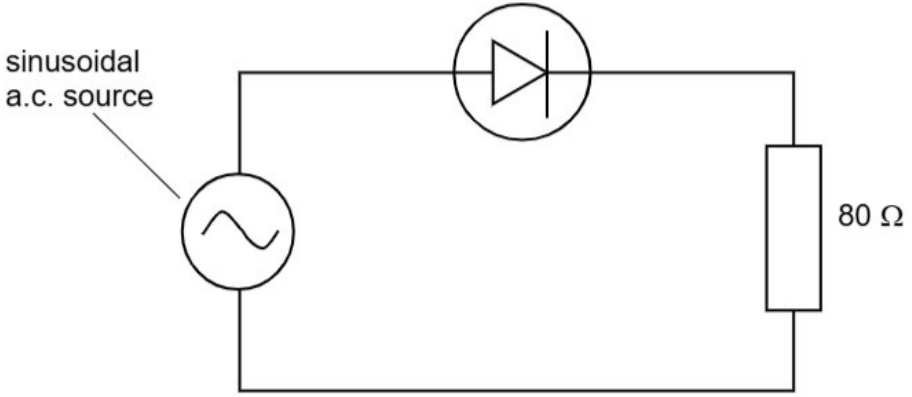

What is the r.m.s. current through the 80 Ω resistor?

A 0.056 A **B** 0.080 A **C** 0.11 A **D** 0.16 A