23 A network of capacitors, all of the same capacitance C, is connected to a cell as shown.

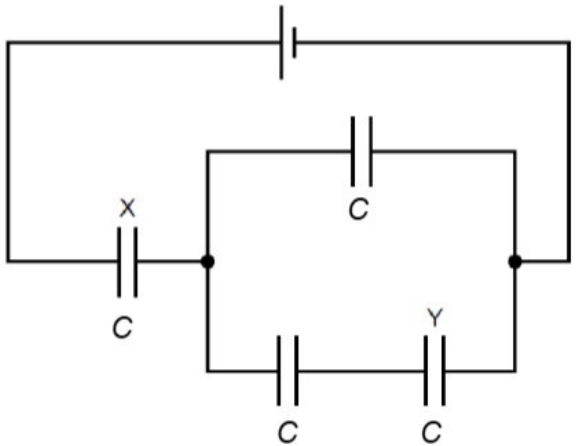

The potential difference across capacitor X is V.

What is the potential difference across capacitor Y?

A $\frac{V}{3}$ **B** $\frac{2V}{3}$ **C** $\frac{3V}{4}$ **D** $\frac{3V}{2}$