
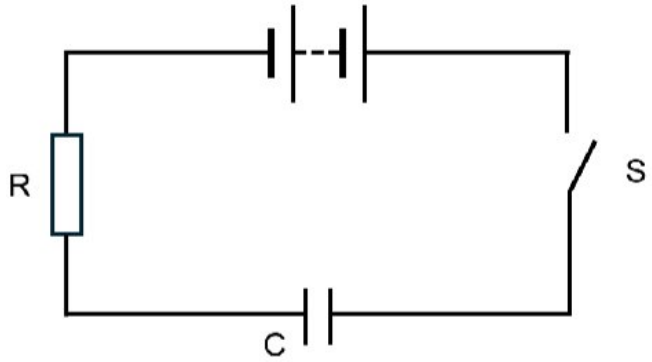
24 An uncharged capacitor C is connected in series to a battery, resistor R and a switch S.




Which of the following graphs shows the variation with time *t* of the power *P* dissipated in the resistor when switch S is closed ?


A

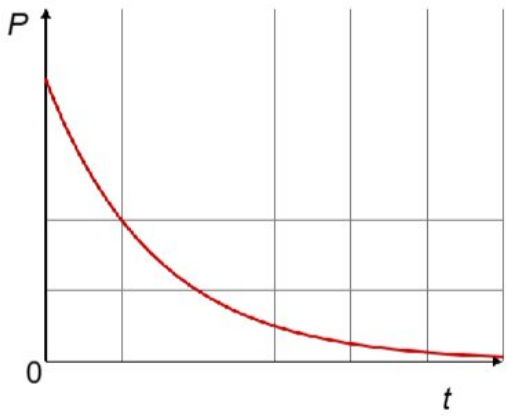

B

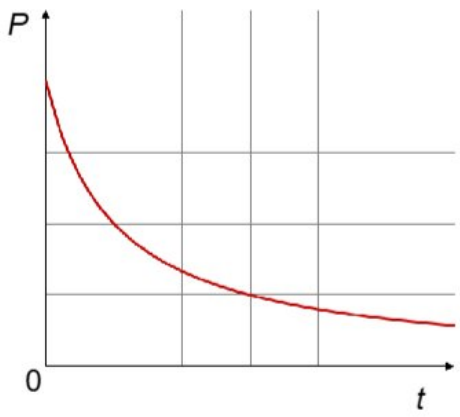

C

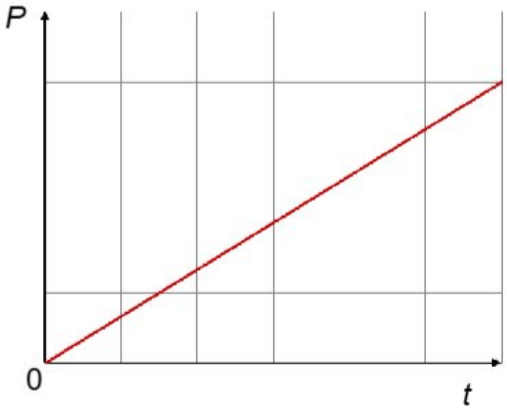

D

