21 A circuit is needed to turn on a heater when the temperature of a thermistor is too low.

Which of the following circuits is suitable?

A

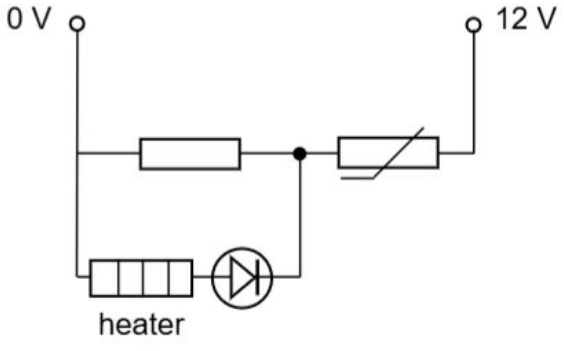

B

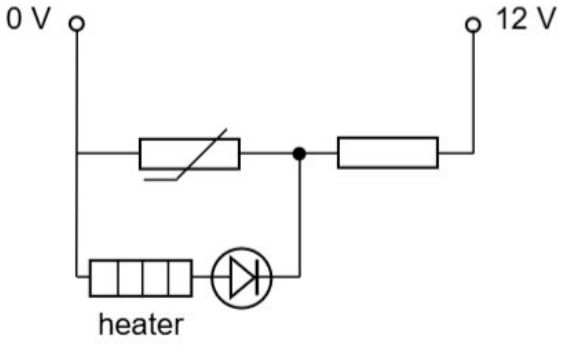

C

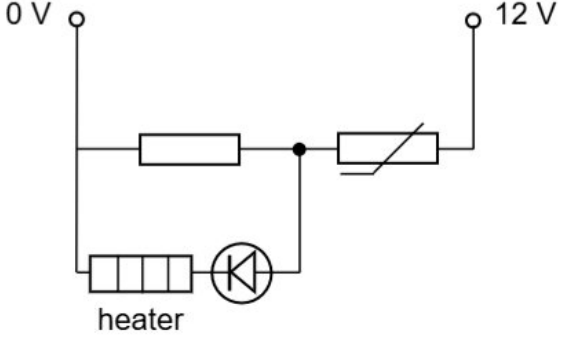
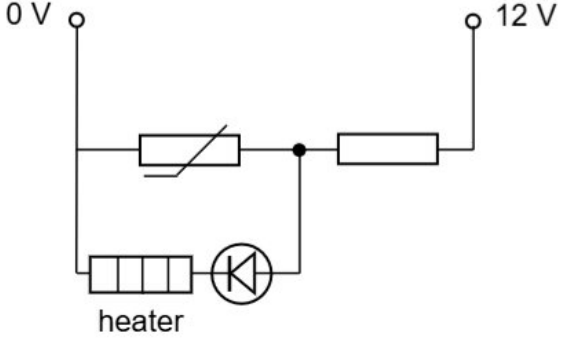
D