26 The graph shows an alternating current with a square waveform.

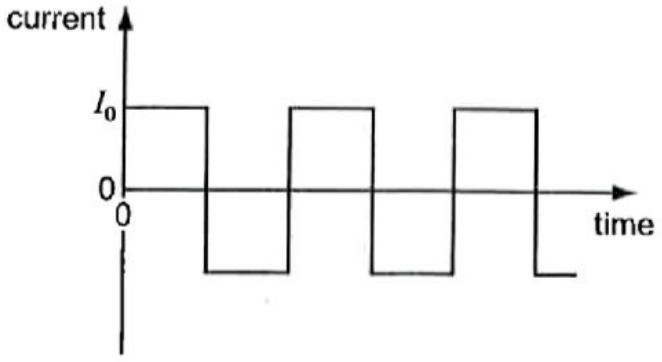

The peak value of the current is I_0 and the average power dissipated in the circuit is given by P.

What is the new average power dissipated if the peak value is now doubled to $2I_0$?

A P **B** 1.4 P **C** 2 P **D** 4 P