22 A capacitor is charged by a constant current of 2.5 μA for 200 s. As a result, the potential difference across the capacitor increases by 5.0 V.

What is the capacitance of the capacitor?

A 40 μF **B** 100 μF **C** 40 mF **D** 100 mF