23 Six identical capacitors, each of value C, are connected as shown.

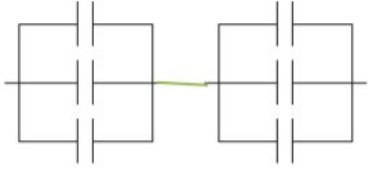

What is the total capacitance?

A $\frac{1}{6}C$ **B** $\frac{2}{3}C$ **C** $\frac{3}{2}C$ **D** $6C$