22 5 identical resistors of resistance 1.0 Ω are arranged between points A and B as shown below.

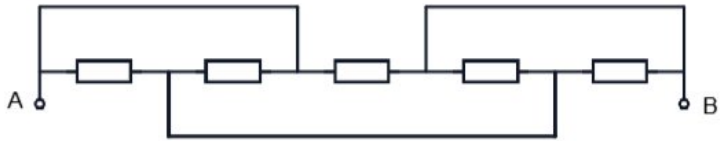

What is the effective resistance between points A and B?

A 0.50 Ω

B 1.0 Ω

C 1.5 Ω

D 5.0 Ω