
25 In the circuit shown below, the switch is initially open and the variable resistor is set to its maximum resistance. The switch is closed quickly.

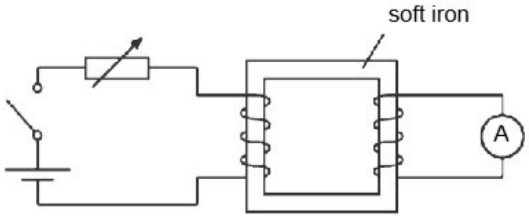The resistance of the variable resistor is then gradually decreased to its minimum value, after which the switch is opened quickly.



At which stage is the magnitude of the current through the ammeter greatest?

A immediately after the switch is closed

B while the resistance is being decreased

C when the resistance reaches its minimum value

D immediately after the switch is opened