22 In the circuit shown, a wire of resistance 100 Ω is used to make a connection between points X and Y.

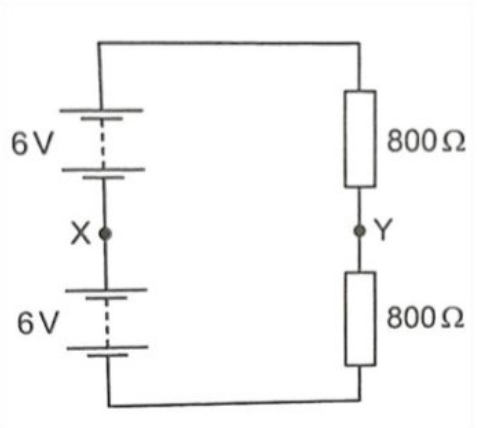

What is the current in this wire?

A 0 **B** 6.7 mA **C** 7.5 mA **D** 60 mA