23 A 20 μF capacitor is charged by a constant current of 10 mA.

If the capacitor is initially uncharged, how long does it take for the potential difference across the capacitor to reach 300 V?

A 6.0×10^{-4} s **B** 0.60 s **C** 15 s **D** 1.5×10^{4} s