27 The root mean square (rms) current in the primary coil of an ideal transformer is 2.0 A. The rms voltage in the secondary coil is 50 V. The average power transferred from the secondary coil is 20 W.

What is N_p/N_s and what is the average power transferred from the primary coil?

	N_p/N_s	Average power transferred from the primary coil / W
A	1 / 5	4.0
B	5	20
C	1 / 5	20
D	5	100